

**Powers of Two:**  $2^0=1, 2^1=2, 2^2=4, 2^3=8, 2^4=16, 2^5=32, 2^6=64, 2^7=128, 2^8=256, 2^9=512, 2^{10}=1024, 2^{11}=2048, 2^{12}=4096, 2^{13}=8192, 2^{14}=16384, 2^{15}=32768, 2^{16}=65536$


Hexadecimal Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

**Number Conversion: D→B:** 1. Determine the largest power of 2 that fits into the number. 2. Then represent the difference with the largest power of 2 that fits into the difference of the two numbers. Repeat steps 1-2. 3. For the powers of 2 that weren't needed, treat them as 0s, and the rest as 1s.

**B→D:** 1. Expand the binary code as the full sum. 2. Add up all the terms.

**B→H:** 1. Group the bits in 4s from R-to-L. 2. Add zeros at the left if doesn't make group of 4.

**Gates:**

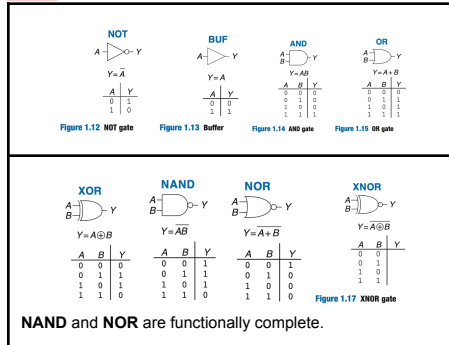

NAND and NOR are functionally complete.

**SOP:** an OR of ANDs. Any SOP circuit can be implemented as NAND.

**Minterm:** Product term that outputs to 1 for exactly 1 row of TT.  $x_i$  if  $x_i=1$  &  $\bar{x}_i$  if  $x_i=0$ .

**POS:** AND of ORs. Any POS circuit can be implemented as NOR.

**Maxterms:** Sum term that outputs to 0 for exactly 1 row of TT.  $x_i$  if  $x_i=0$  &  $\bar{x}_i$  if  $x_i=1$ .

-Anytime we need to implement NOR or NAND, use DeMorgans.

**Implicant:** Any product term included by f.

**PI:** An implicant for which it is not possible to remove any literal and still have a valid implicant. The **largest group of 1s which can be circled** to cover the particular 1 in K-map.

**Cover:** Any set of implicants that includes all minterms of a function.

**EPI:** A PI that covers at least one minterm that is not covered by any other PI.

**Procedure for Finding a Min. Cost Cover:**

1. Find PIs and identify EPIs (include in cover)
2. Choose other PIs as needed until all minterms are covered, such that the number of literals is minimized. There can be **\*\*multiple min. cost covers\*\***.

$$\text{Cost} = \# \text{ gates} + \# \text{ inputs}$$

**K-Map:**

1. Use the fewest circles necessary to cover all the 1's.
2. All the squares in each circle must contain 1's.
3. Each circle must span a rectangular block that is a power of 2 squares in each direction.
4. Each circle should be as large as possible.
5. A circle may wrap around the edges of the K-map.
6. A 1 in a K-map may be circled multiple times if doing so allows fewer circles to be used.


**Don't Cares (d):** Each don't care minterm can arbitrarily be 0 or 1.

**Multiplexers/Decoders:**


Mux chooses an output from among several possible inputs, based on the value of a **select** signal. If  $s=0$ , then f is controlled by x, else y.

2:1 mux - selects 1 of 2 possible inputs

 4:1 mux - select 1 of 4 possible inputs (s would be two bits)



Mux with 2-bit inputs x, y

 

**Verilog Syntax:**

Op	Meaning
H	~ NOT
i	*, /, % MUL, DIV, MOD
g	+, - PLUS, MINUS
h	<<, >> Logical Left/Right Shift
e	<<<, >>> Arithmetic Left/Right Shift
s	<, <=, >, >= Relative Comparison
t	==, != Equality Comparison
L	&, ~& AND, NAND
o	^, ~^ XOR, XNOR
w	, ~  OR, NOR
c	?: Conditional

**Mux 2-to-1:**

```
module mux2to1(input logic x, y, s, output logic f);
    assign f = (~s & x) | (s & y);
endmodule
```

```
module mux2to1_2bits(input logic [1:0] x, y, input logic s, output logic [1:0] f);
    assign f[1] = (~s & x[1]) | (s & y[1]);
    assign f[0] = (~s & x[0]) | (s & y[0]);
endmodule
```

**Simplifying Equations:**

- Expanding an implicant ( $AB=ABC+AB\bar{C}$ ) useful to be shared with another minterm.
- Use distributive to expand out POS into SOP.
- Duplicate terms using idempotency.
- Check: **\*\*Perfect Induction\*\*** ( $LS=RS$ )

**Half Adder**

```
module HA(input logic a, b, output logic [1:0] s);
    assign s[1] = a & b;
    assign s[0] = a ^ b;
endmodule
```

**Full Adder**

```
module FA(input logic a, b, cin, output logic s, cout);
    assign s = a ^ b ^ cin;
    assign cout = (a & b) | (cin & a) | (cin & b);
endmodule
```

**Hierarchical Verilog Code**


```
module adder3(input logic [2:0] A, B, input logic cin,
    output logic [2:0] S, output logic cout);
    logic C1, C2; //internal signals
    FA = u0(A[0], B[0], cin, S[0], C1);
    FA = u1(A[1], B[1], C1, S[1], C2);
    FA = u2(A[2], B[2], C2, S[2], cout);
endmodule
```

**Segment 7**

```
module seg7(input logic [0:1] x, output logic [6:0] H);
    assign H[0] = ~x[1] & x[0];
    assign H[1] = 1'b0; // sets 1 bit to be 0.
    assign H[2] = x[1] & ~x[0];
    assign H[3] = ~x[1] & x[0];
    assign H[4] = x[0];
    assign H[5] = x[1] | x[0];
    assign H[6] = ~x[1];
endmodule
```

**Latches:**

 
**RS Latch (Left) & Characteristic Table (Right):**



Inputs S (set) & R (reset), Outputs Q &  $\bar{Q}$



 **Gated RS Latch (Clock Input to Dis./Ena. Latch):**



^ Cheaper implementation.


-If  $\text{Clk}=0$ , retain previous value. If  $\text{Clk}=1$ , use R and S.

-When  $\text{Clk}=0$ , both R' & S' are 0 & the latch is storing the value. Only when  $\text{Clk}$  is 1, can value be set or reset.

-Problem w/ RS Latch, it can oscillate when  $R, S=1$  to  $R, S=0$ .

 **Gated D Latch:**

Let  $S = D, R = \bar{D}$ , where D is the data input  $\Rightarrow$  Impossible to have a situation where  $R=S=1$ .




-When  $\text{clk}=1, Q=D$

-When  $\text{clk}=0, Q$  will store the present value of D.



 
### Flip-Flops (Positive Edge Triggered FF):


-C1:  $\text{Clk}=0$ ;  $Q_n=0$ ,  $Q=0/1$  (stored value)  
 -C2:  $\text{Clk}$  ("posedge"):  $Q=Q_n=D$  (no longer tracks input changes).  
 So when  $\text{Clk}$  changes from 0 to 1, the value of  $D$  at that moment is stored in FF.




 
**Resets and Enables:** Need to reset FF to known value  
**Resetn:** Active low reset (corresponds w/ 0)  
**Synchronous (with clock edge):**


 
```
module D_FF(input logic D, Clk, resetn, output logic Q);
  always_ff @(posedge Clk) // at clk edge
    if (resetn==0) // active low reset
      Q<=1'b0; // Q set to 1 bit as 0.
    else
      Q<=D;
endmodule
```


  
### Difference Gated D-Latch, Posedge FF, Negedge FF



**Register:** Synonym for FF.

### Verilog for D-Latch:

```
module D_Latch(input logic D, clk, output logic Q);
  always_latch
    if (clk==1)
      Q=D;
endmodule
```

// the latch stores Q when clk is not 1.

**Note:** If code does not specify the value of a signal in some conditions, the compiler will insert a latch to store the value of that signal.

### Verilog for FFs:


```
module D_FF(input logic D, Clk, output logic Q);
  always_ff @(posedge clk) // (?) is sensitivity list.
    Q<=D; // <= is an assignment op.
endmodule
```

-Any signal assigned a value inside an always block using posedge becomes Q output of a FF.  
 -When code describes FFs, the assignments should use <=
 
### Verilog for Register:

```
module reg8(input logic [7:0] D, input logic clk, output logic [7:0] Q);
  always_ff @(posedge clk)
    Q<=D;
endmodule
```

**Enable Input:** Determine whether data is load on clock edge.




-Passes new value D to FF if  $E_n=1$ , otherwise recycles old state.

### FSM:

1. State diagram
  2. State-table
  3. State assignment (ie. Choose # FFs, and state codes)
  4. State-assigned table
  5. Synthesize the circuit
- # of FFs & how we define the states is what we changed.

 
### Asynchronous (Independent of clock edge):



-C1: If  $\text{Clk}=0$ ,  $\text{resetn}=0$ , gives  $Q = 0$ ,  $\bar{Q} = 1$   
 -C2: If  $\text{Clk}=1$ ,  $\text{resetn}=0$ , gives  $Q = 0$ ,  $\bar{Q} = 1$   
 -Proves that this is independent of the clock edge.

```
module D_FF(input logic D, clk, resetn, output logic Q);
  always_ff @(posedge clk, negedge resetn)
    if (resetn==0)
      Q<=1'b0;
    else
      Q<=D;
endmodule
```

 -resetn in sensitivity list b/c it can directly affect Q



### Multi-bit Register With Synchronous Reset

```
module reg8(input logic [7:0] D, input logic resetn, clk, output logic [7:0] Q);
  always_ff @(posedge clk)
    if (resetn==0)
      Q<=8'b0;
    else
      Q<=D;
endmodule
```

### Verilog Code for FSMs:

```
1. FFs, 2. State-table, 3. Output
module FSM(input logic w, clock resetn, output logic z);
  typedef enum logic [1:0] (A,B,C,D) statetype;
  // typedef defines statetype to be 2bit logic values
  // ps,ns are 2-bit and can take A-D.
  // enumerated encodings default to numerical
  // A=00, B=01, C=10, D=11
  statetype ps,ns;
  // FFs
  always_ff @(posedge clock, negedge resetn)
    if (!resetn) ps <= A;
    else ps <= ns;

  // State Table
  always_comb
    case(ps) // change cases on ps
      A: if (w) ns = B;
        else ns = A;
      B: if (w) ns = B;
        else ns = A;
      C: if (w) ns = D;
        else ns = A;
      D: if (w) ns = B;
        else ns = C;
    endcase

  // Output
  assign z = (ps==D); // z is 1 when ps is D.
endmodule
```